

# AC to DC Converters


Diego Trapero

## Table of contents

<b>1</b>	<b>AC to DC Converters, Rectifiers</b>	<b>2</b>
<b>2</b>	<b>Monophasic Rectifiers</b>	<b>3</b>
2.1	Half Wave Rectifier . . . . .	3
2.2	Full Wave Rectifier . . . . .	4
2.2.1	R Load . . . . .	6
2.2.2	RC Load . . . . .	6
2.2.3	RLC Load . . . . .	8
2.2.4	RL load . . . . .	10
2.2.5	Controlled Full Wave Rectifier R . . . . .	10
2.2.6	Controlled Full Wave Rectifier RL . . . . .	11
2.2.7	Controlled Full Wave Rectifier RLE . . . . .	14
<b>3</b>	<b>Triphasic Rectifiers</b>	<b>15</b>
3.1	Half Wave Triphasic Rectifier . . . . .	15
3.2	Full Wave Triphasic Rectifier . . . . .	15
<b>4</b>	<b>Reference</b>	<b>15</b>

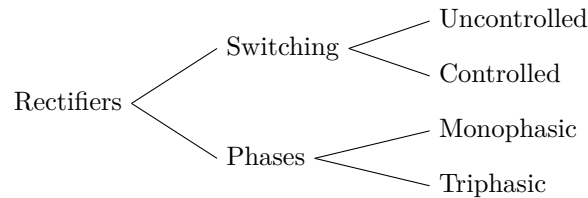
# 1 AC to DC Converters, Rectifiers

A AC/DC Converter, or rectifier, is an electrical device that converts alternating current (AC), which periodically reverses direction, to direct current (DC), which flows in only one direction. Physically, rectifiers take a number of forms, including vacuum tube diodes, mercury-arc valves, copper and selenium oxide rectifiers, semiconductor diodes, silicon-controlled rectifiers and other silicon-based semiconductor switches. Historically, even synchronous electromechanical switches and motors have been used. #




- Uncontrolled rectifiers use diodes as switching devices. They don't need a control circuit.


## Diodes

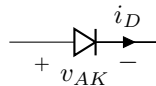

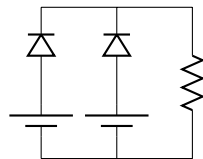**Common Cathode Diodes** If two or more diodes are connected with a common cathode, the closed diode is the one with the most positive anode voltage. The rest of the diodes are open.



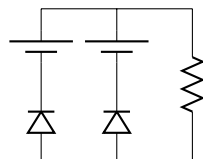**Common Anode Diodes** If two or more diodes are connected with a common anode, the closed diode is the one with the most negative anode voltage. The rest of the diodes are open.



Configuration	Circuit diagram	Conducting Diode
Common Cathode		The diode with the most positive anode voltage
Common Anode		The diode with the most negative cathode voltage

General rule: The most polarized diode is the one conducting. The one with the biggest  $v_{AK}$


## Thyristors

(Ideal)

- Closing conditions
  - $v_A K > 0$ , the thyristor is forward polarized
  - $i_G$ , current in the gate (thyristors are current-controlled)
- Opening conditions
  - $i_A K < 0$ , current is reversed


## 2 Monophasic Rectifiers

### 2.1 Half Wave Rectifier

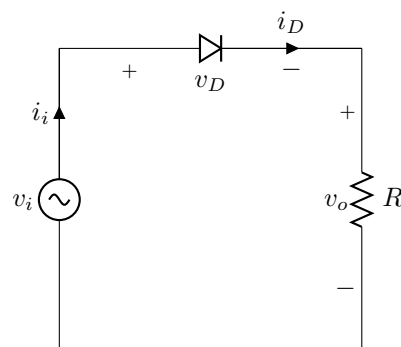


- $v_i > 0$  : D ON,  $i > 0$
- $v_i < 0$  : D OFF,  $i = 0$


$v_i > 0$  (D ON) equivalent circuit

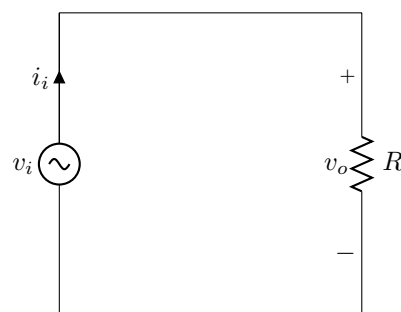

$v_i < 0$  (D OFF) equivalent circuit

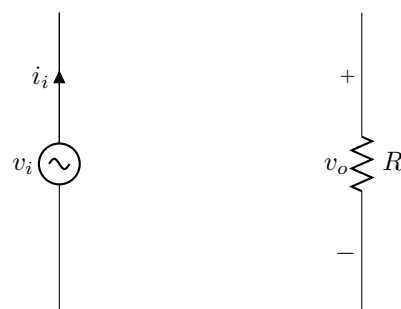


Output voltage,  $v_o$

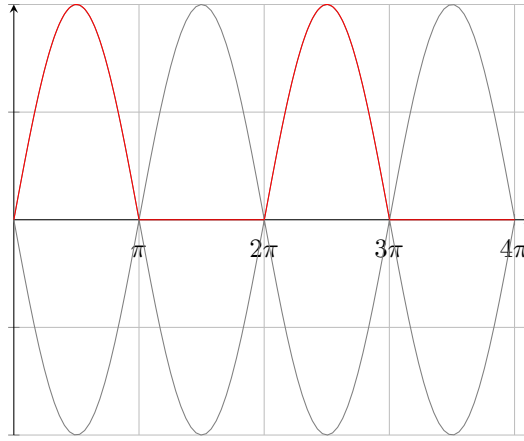

The voltage in the resistive load,  $v_R$ , and the current demanded to the source depends on the load type, and can be different for a same kind of rectifier depending on the load that is connected to it.


## 2.2 Full Wave Rectifier

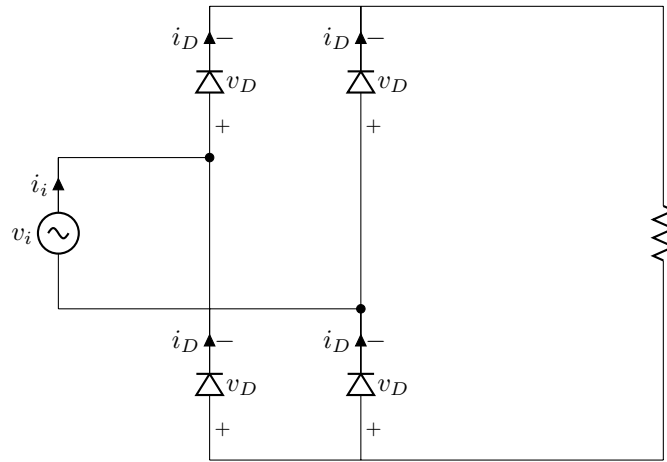

where

- $v_i$  is a pure sinusoidal wave  $v_i = V_i \sqrt{2} \sin(2\pi f)$ 
  - RMS value is  $V_i$
  - Peak value, or  $V_{ip}$  is  $V_i \sqrt{2}$
  - Frequency is  $f$
  - $\varphi = 0$  because it is the reference for phase shifts
- $R$  is resistance that models the load


### Full Wave Rectifier Symbol

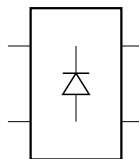


### Diode table

	D1	D2	D3	D4
$v_i > 0$	ON	OFF	OFF	ON
$v_i < 0$	OFF	ON	ON	OFF

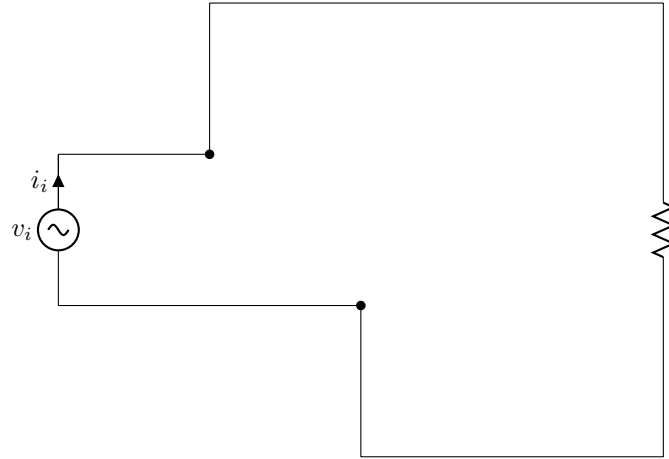
$v_i > 0$  **equivalent circuit:** D1, D4 are ON



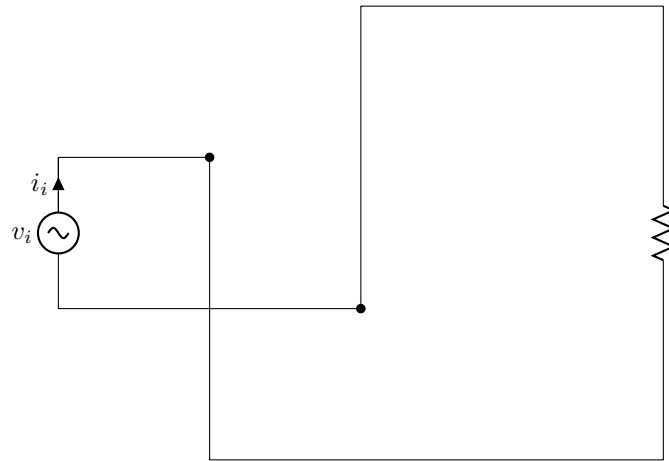$v_i < 0$  **equivalent circuit:** D2, D3 are ON



**Output voltage,  $v_o$**

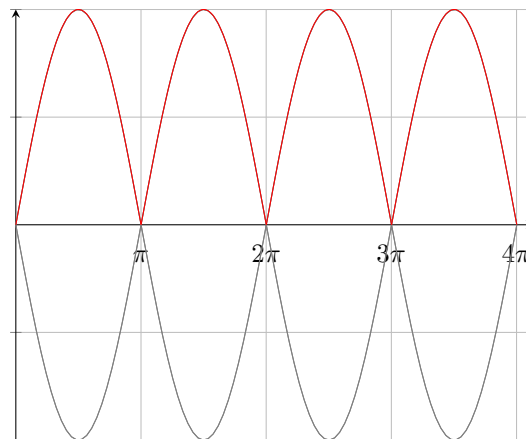


The voltage in the resistive load,  $v_R$ , and the current demanded to the source depends on the load type, and can be different for a same kind of rectifier depending on the load that is connected to it.


*Note:* Although this  $v_o$  waveform can always be used with the reduced model circuit, where it is behind a diode, in some cases, like the RC load, the  $v_o$  node in the complete circuit coincides with the  $v_R$  node and the output voltage directly after the rectifier has not this typical rectified waveform, but a filtered version of it.

**Reduced model of the rectifier** If  $v_o$  is already known, a simplified model of the rectifier can be represented to study the loaded rectifier. The left hand side of the circuit is substituted by

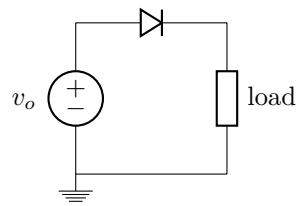- a  $v_o$  voltage source, that represents the bridge output voltage
- a diode that represents that current cannot enter in the rectifier




### 2.2.1 R Load

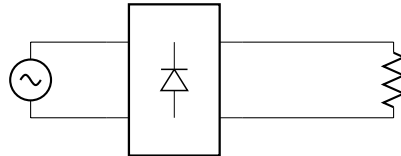

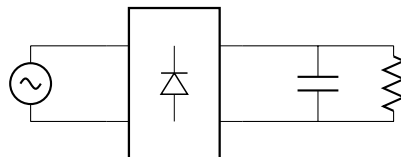
### 2.2.2 RC Load

A condenser can be added in parallel with the R load to smooth the voltage across it. In this case, the circuit is




**Output voltage,  $v_o$ ; Load voltage,  $v_R$**

- Mean value

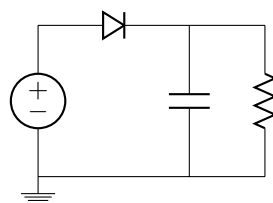

*Not exactly like this, it's more complex.*

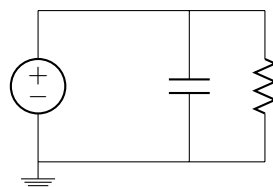
- When the diode conducts,  $v_o = v_R$  and the capacitor is charged with the current from the source.



The charge is sinusoidal:

$$i_C(t) = \frac{dv(t)}{dt} = \text{sinusoidal}$$

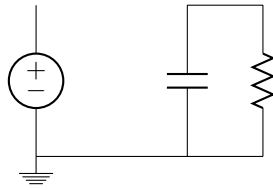
- When the diode is not conducting, the capacitor provides the current to the load. It would continue to discharge until  $v_o = v_i$ .



The discharge is exponential:


*formulita*

The voltage in the load is:

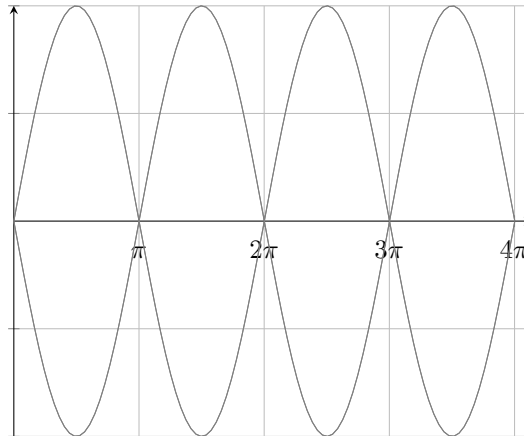
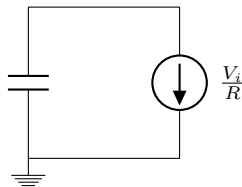
### Triangular approximation

- The charge is considered instantaneous:  $t_{\text{charge}} = 0 \rightarrow t_{\text{discharge}} = \frac{T}{2}$
- The discharge is linear, with constant current:  $I_R = V_m/R$
- The diode opens in the maximum of  $v_o$ :  $I_R = V_i/R$  (in the slides it says “if ripple is small enough”).



The ripple of the wave using the triangular approximation is

$$\Delta v_o = \frac{V \Delta T}{C}$$

$$\Delta v_o = \frac{V_i T}{2RC}$$

**Mean value** Can be calculated from the triangular approximation

$$\bar{v}_o = V_{ip} - \frac{1}{2} \Delta v_o$$


### Advantages of a smoothing condenser

- Small size
- Cheap
- Robust

## Disadvantages of a smoothing condenser


- High peaks of current through the diodes.
- Harmonics in the source current.
- Need of a big capacitor if the required ripple is small.

### 2.2.3 RLC Load

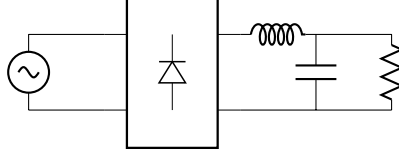


$v_R$  **mean value**

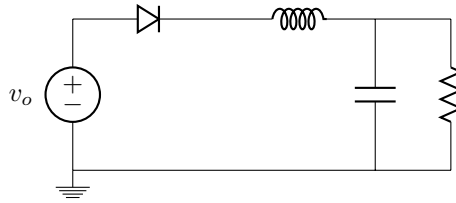The mean value of  $v_o$  can be calculated by using superposition with the circuit:



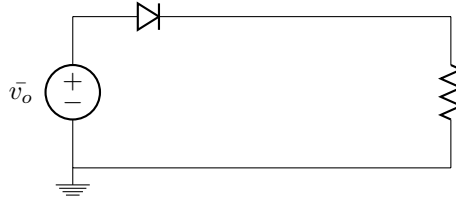For the mean values, the resulting DC circuit is:



The resulting  $\bar{v}_R$  is

$$\bar{v}_R = \bar{v}_o = \frac{2V_{ip}}{\pi}$$

**RLC circuit transfer function**

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{1 + \frac{L}{R}j\omega - LC\omega^2}$$

$$H = \left| \frac{\mathbf{V}_o}{\mathbf{V}_i} \right| = \frac{1}{\sqrt{(1 - LC\omega^2)^2 + (\frac{L}{R}\omega)^2}}$$

$v_R$  **ripple**

Ripple is due to the first harmonic:

$$\Delta v_R = H_{filter} \cdot |V_{o1}|$$

$$H = \frac{1}{\sqrt{(1 - LC\omega^2)^2 + (\frac{L}{R}\omega)^2}}$$


$$|V_{o1}| = \frac{4}{\pi} \frac{1}{3} V_{ip}$$

**Inductor current,  $i_L$**

Inductor current can be approximated with its mean value and ripple.




- **Mean value.** Using superposition

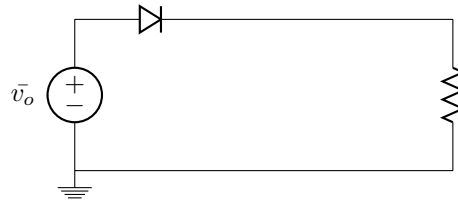

$$i_L = \frac{\bar{v}_o}{R}$$

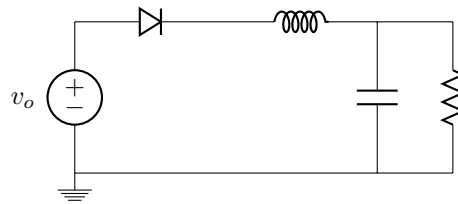- **Ripple.** As in the  $v_R$  ripple, maximum variation of the current is due to the 1st harmonic of  $v_o$ . Thus, ripple can be calculated:



$$I_{1p} = \frac{V_{o1}}{Z_1}$$


If  $\Delta v_R$  is already calculated, it can be used to compute the ripple:

$$\Delta i_L = \frac{\Delta v_R}{Z_{RC}}$$

The rectifier is in CCM if the inductor is always conducting some current:

$$\frac{1}{2}\Delta i_L < \bar{i}_L$$

**Power factor in the source**

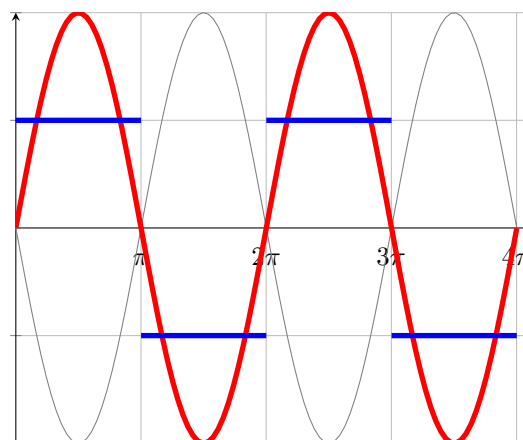

$$\text{PF} = \frac{P}{S}$$

- Only first harmonic delivers power:

$$P = V_1 I_1 \cos(\varphi)$$

$$P = \frac{V_{ip}}{\sqrt{2}} \frac{4}{\pi} \frac{I_o}{\sqrt{2}} \cos(\alpha)$$

- Apparent power

$$S = V_{\text{RMS}} I_{\text{RMS}}$$

$$S = \frac{V_{ip}}{\sqrt{2}} I_o$$

$$\text{PF} = \frac{P}{S} = \frac{\frac{V_{ip}}{\sqrt{2}} \frac{4}{\pi} \frac{I_o}{\sqrt{2}} \cos(\alpha)}{\frac{V_{ip}}{\sqrt{2}} I_o}$$

$$\text{PF} = \frac{4}{\pi} \frac{1}{\sqrt{2}} = \frac{2\sqrt{2}}{\pi} \cos(\alpha)$$

### Advantages of LC filtering

- No current peaks in the diodes.
- Less condenser ripple.
- Less capacity and current capacitor required.


### Disadvantages of LC filtering

- Size and weight of the inductor

#### 2.2.4 RL load


#### Flyback Diode
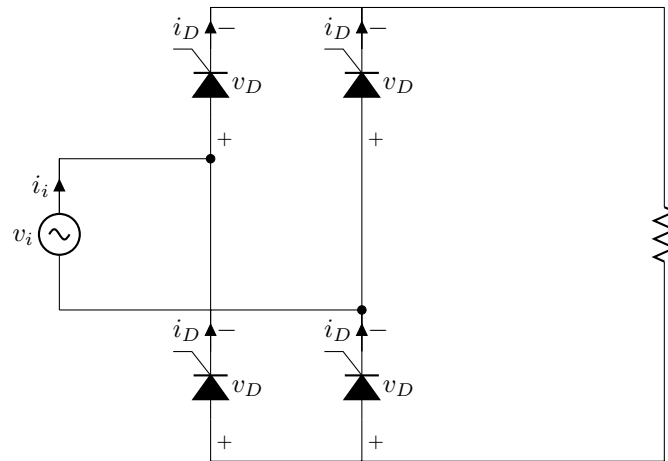
#### 2.2.5 Controlled Full Wave Rectifier R



where

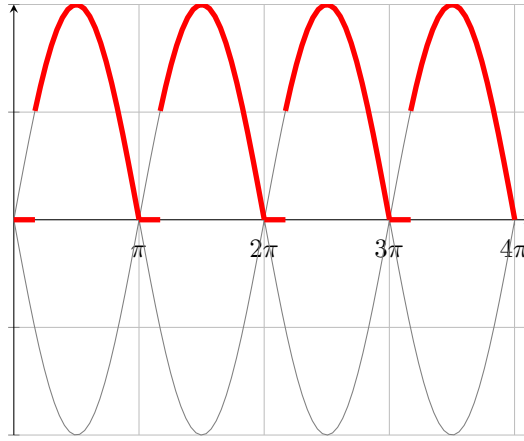- $v_i$  is a pure sinusoidal wave  $v_i = V_i \sqrt{2} \sin(2\pi f)$ 
  - RMS value is  $V_i$
  - Peak value, or  $V_{ip}$  is  $V_i \sqrt{2}$
  - Frequency is  $f$
  - $\varphi = 0$  because it is the reference for phase shifts
- $R$  is resistance that models the load
- $\alpha$  is the delay angle for thyristors





$v_o$  mean value,  $\bar{v}_o$

$$\begin{aligned}
 \bar{v}_o &= \frac{1}{T} \int_{\theta_0}^{\theta_0+T} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_0^{\pi} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_0^{\alpha} 0 d\theta + \frac{1}{\pi} \int_{\alpha}^{\pi} V_{ip} \sin(\theta) d\theta \\
 &= \frac{V_{ip}}{\pi} [-\cos(\theta)]_{\alpha}^{\pi} \\
 &= \frac{V_{ip}}{\pi} [-\cos(\pi) + \cos(\alpha)] \\
 &= \frac{V_{ip}}{\pi} (\cos(\alpha) + 1)
 \end{aligned}$$
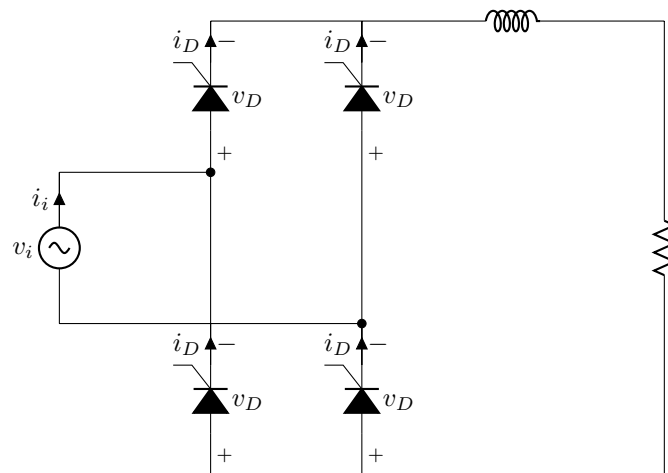
### 2.2.6 Controlled Full Wave Rectifier RL

When it is loaded with a RL load, current cannot be suddenly cut and thyristors continue to be closed even when they're polarized backwards, until the other branch is triggered. The



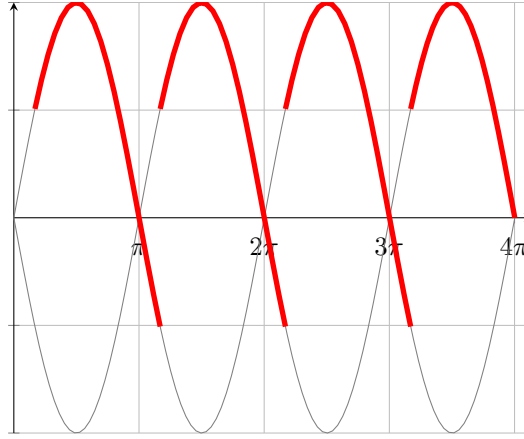

$v_o$  mean value,  $\bar{v}_o$

$$\begin{aligned}
 \bar{v}_o &= \frac{1}{T} \int_{\theta_0}^{\theta_0+T} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_{ip} \sin(\theta) d\theta \\
 &= \frac{V_{ip}}{\pi} [-\cos(\theta)]_{\alpha}^{\alpha+\pi} \\
 &= \frac{V_{ip}}{\pi} [-\cos(\alpha + \pi) + \cos(\alpha)] \\
 &= \frac{2V_{ip}}{\pi} \cos(\alpha)
 \end{aligned}$$

$\bar{v}_o$  with flyback diode Same as R loaded converter


$$\begin{aligned}
 \bar{v}_o &= \frac{1}{T} \int_{\theta_0}^{\theta_0+T} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_0^{\pi} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_0^{\alpha} 0 d\theta + \frac{1}{\pi} \int_{\alpha}^{\pi} V_{ip} \sin(\theta) d\theta \\
 &= \frac{V_{ip}}{\pi} [-\cos(\theta)]_{\alpha}^{\pi} \\
 &= \frac{V_{ip}}{\pi} [-\cos(\pi) + \cos(\alpha)] \\
 &= \frac{V_{ip}}{\pi} (\cos(\alpha) + 1)
 \end{aligned}$$

**Phases** *hacer mejor, poner circuiticos, explicar por que se extingue la corriente a traves de los tiristores*

1.  $v_i > 0$ , T1 and T4 triggered
  - T2 and T3 are backwards polarized
  - T1 and T4 have been triggered and are conducting
  - $i_i > 0$
2.  $v_i < 0$ , T2 and T3 haven't been triggered yet
  - T2 and T3 are forward polarized but haven't been triggered yet
  - T1 and T4 are still conduction because current through the inductor cannot be discontinued
  - $i_i > 0$
3.  $v_i < 0$ , T2 and T3 triggered

- T1 and T4 are triggered and start conducting.
  - Current extinguishes through T2 and T3, that cur and become backwards polarized
  - $i_i < 0$
4.  $v_i > 0$ , T2 and T3 haven't been triggered yet
- $i_i < 0$

**Source current,  $i_i$**

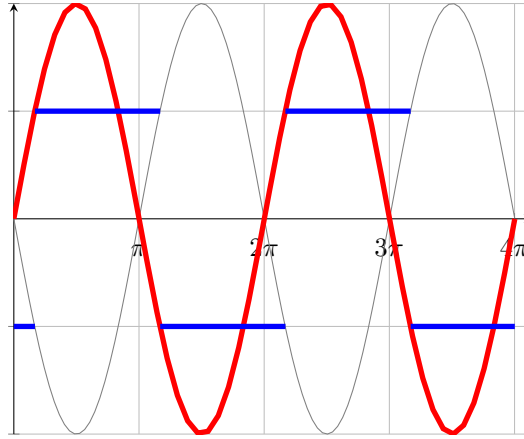

*Tip:* For drawing the current, when the thyristors are triggered during the positive semicycle of the  $v_i$  current, current flows in the positive direction. Or,  $\alpha$  delays the current square wave.

### Power

Calculated in the source:

Only first harmonic produces power:

$$P = V_{1RMS} I_{1RMS} \cos(\varphi_1)$$

$$P = \frac{V_{ip}}{\sqrt{2}} \frac{4}{\pi} \frac{I}{\sqrt{2}} \cos(\alpha)$$

$$P = \frac{2V_{ip}I}{\pi} \cos(\alpha)$$

**Power factor in the source**

$$\text{PF} = \frac{P}{S}$$

$$P = \frac{2V_{ip}I}{\pi} \cos(\alpha)$$



$$S = V_{RMS} I_{RMS}$$

$$S = \frac{V_{1p}}{\sqrt{2}} I$$

$$\text{PF} = \frac{P}{S} = \frac{2\sqrt{2}}{\pi} \cos(\alpha)$$
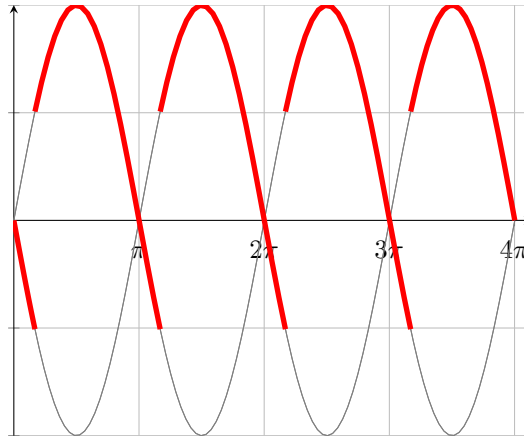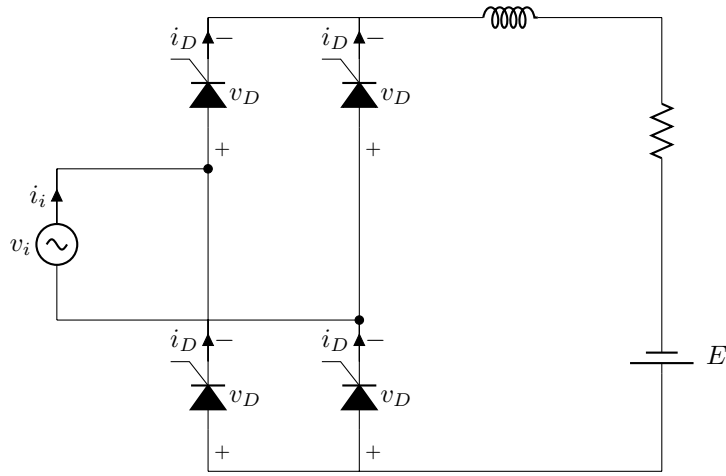
### 2.2.7 Controlled Full Wave Rectifier RLE


RLE loads can be used to transfer power to the net, for example in solar powers. Using a rectifier to inject power in the net is cheaper than using an inverter because it uses thyristors instead of MOSFETs/IGBTs, which are more expensive.



$v_o$  mean value,  $\bar{v}_o$

$$\begin{aligned}
 \bar{v}_o &= \frac{1}{T} \int_{\theta_0}^{\theta_0+T} v_o(\theta) d\theta \\
 &= \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_{ip} \sin(\theta) d\theta \\
 &= \frac{V_{ip}}{\pi} [-\cos(\theta)]_{\alpha}^{\alpha+\pi} \\
 &= \frac{V_{ip}}{\pi} [-\cos(\alpha + \pi) + \cos(\alpha)] \\
 &= \frac{2V_{ip}}{\pi} \cos(\alpha)
 \end{aligned}$$

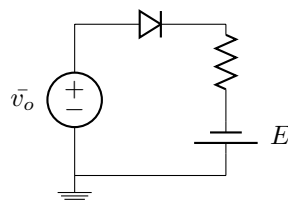**Power flow** Three operating regions, depending of the value of  $\bar{v}_o$ :



$$i = \frac{\bar{v}_o - (-E)}{R}$$

- if  $i > 0$ 
  - if  $\bar{v}_o > 0$ 
    - \* The rectifier produces power
    - \* The E source produces power
    - \* R consumes all the power
    - \* Bad operating regime
  - if  $\bar{v}_o < 0$ 
    - \* The rectifier consumes power
    - \* The E source produces power
    - \* R consumes some power
    - \* Good operating regime if you want to inject power in the net
- if  $i = 0$  the diode blocks the current and no power is consumed or generated

So, if you want to inject power from a DC source into the net with a rectifier, the output voltage of the rectifier should be negative, but current must be flowing from it.

The limit angle is calculated from the condition  $i = 0$ :

$$0 = \frac{\bar{v}_o - (-E)}{R}$$

$$\bar{v}_o = -E$$

## 3 Triphasic Rectifiers

### 3.1 Half Wave Triphasic Rectifier

### 3.2 Full Wave Triphasic Rectifier

## 4 Reference

- <https://en.wikipedia.org/wiki/Rectifier>