

# DC to AC converters



Diego Trapero

## Table of contents


<b>1</b>	<b>DC to AC converters</b>	<b>2</b>
1.1	Full bridge circuit . . . . .	2
<b>2</b>	<b>Square wave control</b>	<b>3</b>
<b>3</b>	<b>Phase shift control</b>	<b>3</b>
<b>4</b>	<b>PWM control</b>	<b>3</b>
4.1	Unipolar control . . . . .	3
4.2	Bipolar control . . . . .	3
<b>5</b>	<b>Triphasic inverters</b>	<b>3</b>
<b>6</b>	<b>Inverter amplitudes tables</b>	<b>4</b>

# 1 DC to AC converters

## 1.1 Full bridge circuit

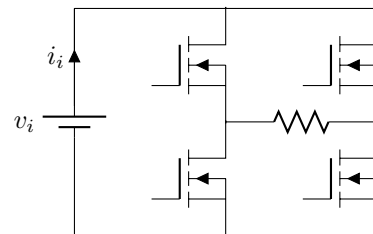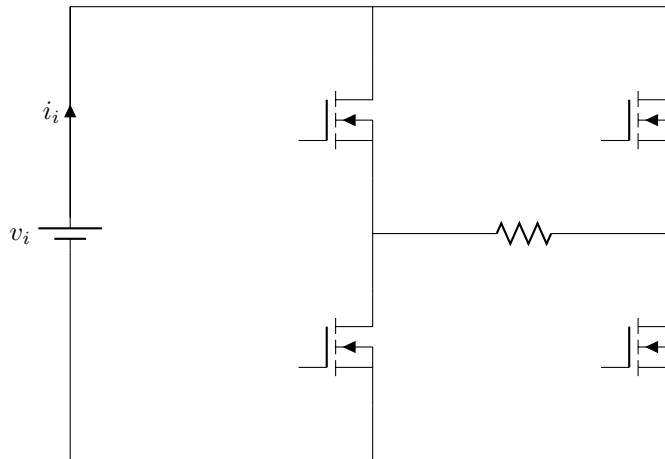


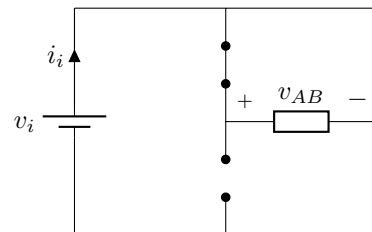**Direct polarization of the load. S1 and S4**





$$v_{AB} = V_i$$

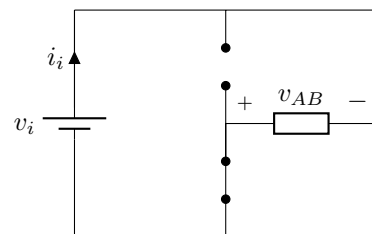**Inverse polarization of the load. S2 and S3**



$$v_{AB} = -V_i$$

**Grounding. S1 and S3 OR S2 and S4**

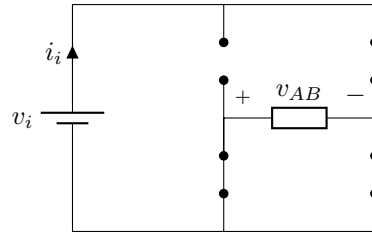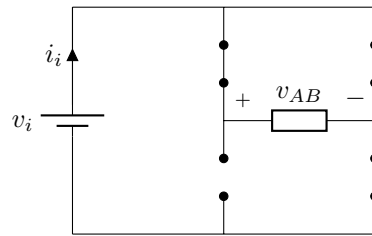

$$v_{AB} = 0$$

**Shorting the source.** The two switches of a branch cannot be closed at the same time because it would short the source. That's the reason why same-branch switch control signals have to be complementary:

$$S1 = \bar{S}3$$

$$S2 = \bar{S}4$$

## 2 Square wave control

## 3 Phase shift control

## 4 PWM control

### 4.1 Unipolar control

### 4.2 Bipolar control

## 5 Triphasic inverters

## 6 Inverter amplitudes tables

**PWM Sinusoidal Unipolar. Normalized amplitudes,  $V_n/V_{DC}$**

$m_a$	0.10	0.20	0.30	0.40	0.50	0.60	0.70	0.80	0.90	1.00
$n = 1$	0.10	0.20	0.30	0.40	0.50	0.60	0.70	0.80	0.90	1.00
$n = 2mf + -1$	0.10	0.19	0.27	0.33	0.36	0.37	0.35	0.31	0.25	0.18
$n = 2mf + -3$	0.00	0.00	0.01	0.02	0.04	0.07	0.10	0.14	0.18	0.21


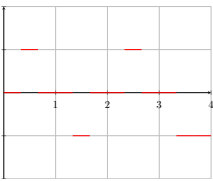
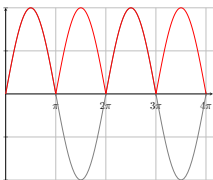
**PWM Sinusoidal Bipolar. Normalized amplitudes,  $V_n/V_{max}$**

$m_a$	0.10	0.20	0.30	0.40	0.50	0.60	0.70	0.80	0.90	1.00
$n = 1$	0.10	0.20	0.30	0.40	0.50	0.60	0.70	0.80	0.90	1.00
$n = mf$	1.27	1.24	1.20	1.15	1.08	1.01	0.92	0.82	0.71	0.60
$n = mf + -2$	0.00	0.02	0.03	0.06	0.09	0.13	0.17	0.22	0.27	0.32

**PWM Sinusoidal Triphasic. Normalized amplitudes,  $V_n/V_{DC}$  (line tension)**

$m_a$	0.10	0.20	0.30	0.40	0.50	0.60	0.70	0.80	0.90	1.00
$n = 1$	0.087	0.173	0.260	0.346	0.433	0.520	0.606	0.693	0.779	0.866
$n = mf + -2$	0.003	0.013	0.030	0.053	0.801	0.114	0.150	0.190	0.232	0.275
$n = 2mf + -1$	0.086	0.165	0.232	0.282	0.313	0.321	0.307	0.272	0.221	0.157

**Fourier series table**

Function	Fourier Series
	$\frac{4}{\pi} \left( \frac{\sin(t)}{1} + \frac{\sin(3t)}{3} + \frac{\sin(5t)}{5} + \dots \right)$
	$\frac{4}{\pi} \left( \frac{\sin(t) \cos(\beta)}{1} + \frac{\sin(3t) \cos(3\beta)}{3} + \frac{\sin(5t) \cos(5\beta)}{5} + \dots \right)$
	$\frac{2}{\pi} - \frac{4}{\pi} \left( \frac{\sin(t)}{1 \cdot 3} + \frac{\sin(2t)}{3 \cdot 5} + \frac{\sin(3t)}{5 \cdot 7} + \dots \right)$