

VHDL

Diego Trapero

Table of contents

1	VHDL syntax	2
1.1	when / else : concurrent signal assignment statement	2
2	Libraries	2
3	Simulation	2
3.1	Clocks	2
3.1.1	Default clock	2
3.1.2	My Clock	3
4	Snippets	3
4.1	Rellenar un vector de ceros	3
4.2	Synchronous processes	3
5	VHDL component	3
5.1	Gates	3
5.2	Biestables	4
5.2.1	Basic D Flip Flop (FD)	5
5.2.1.1	Code	5
5.2.1.2	Synthesis results	5
5.2.1.3	Testbench	7
5.2.1.4	Simulation	8
5.2.2	D Flip Flop with Enable and Asynchronous Reset	8
5.2.2.1	Code	8
5.2.2.2	Synthesis	8
5.2.3	D Flip Flop with Enable, Reset and Preset	10
5.2.3.1	Code	10
5.2.3.2	Synthesis	10
5.3	FSM	11
6	Examples	11
7	More	11

1 VHDL syntax

1.1 when / else : concurrent signal assignment statement

A sequential signal assignment statement is also a concurrent signal assignment statement. Additional control is provided by the use of postponed and guarded.

```
[ label : ] sequential signal assignment statement  
  
[ label : ] [ postponed ] conditional_signal_assignment_statement ;  
  
[ label : ] [ postponed ] selected_signal_assignment_statement ;
```

The optional guarded causes the statement to be executed when the guarded signal changes from False to True. conditional signal assignment statement

A conditional assignment statement is also a concurrent signal assignment statement.

```
target <= waveform when choice; -- choice is a boolean expression  
target <= waveform when choice else waveform;  
  
sig <= a_sig when count>7;  
sig2 <= not a_sig after 1 ns when ctl='1' else b_sig;  
  
-- "waveform" for this statement seems to include [ delay_mechanism ]  
-- See sequential signal assignment statement
```

2 Libraries

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

3 Simulation

3.1 Clocks

3.1.1 Default clock

Default clock used in automatically generated testbenches:

```
constant <clock>_period : time := 10 ns;  
  
-- Clock process definitions  
<clock>_process :process  
begin  
    <clock> <= '0';  
    wait for <clock>_period/2;  
    <clock> <= '1';  
    wait for <clock>_period/2;  
end process;
```

3.1.2 My Clock

```
--proceso de reloj, útil para un testbench

-- inicializar la variable en la zona de señales
SIGNAL CLK  : STD_LOGIC := '0';

clock : process(clk)
begin
    clk <= not clk after 20ns;
end process;
```

4 Snippets

4.1 Rellenar un vector de ceros

```
vector <= (others => '0');
```

4.2 Synchronous processes

Todos los procesos sincronicos con resets

```
--todos los procesos sincronicos con resets:

process (clk, reset)
    if reset = '1' then
        -- do RESET, other asynchronous taska ;
    elseif rising_edge(clk) then
        -- SINCRONOUS TASKS
        if enable = '1' then
            -- ENABLED TASKS

        endif;
    end process;
```

5 VHDL component

5.1 Gates

NAND Gate

```
entity NANDGate is
    port (
        a, b : in bit;
        x : out bit
    );
end NANDGate;

architecture NANDArch of NANDGate is
begin
    x <= a NAND b;
end NANDArch;
```

5.2 Biestables

Latch Internal signal implementation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity S_R_latch_top is
    Port ( S : in    STD_LOGIC;
          R : in    STD_LOGIC;
          Q : out   STD_LOGIC);
end S_R_latch_top;

architecture Behavioral of S_R_latch_top is
    signal Q2    : STD_LOGIC;
    signal notQ  : STD_LOGIC;
begin

    Q    <= Q2;
    Q2   <= R nor notQ;
    notQ <= S nor Q2;

end Behavioral;
```

Latch Inout ports implementation

```
entity SR_Latch is
    Port ( S,R : in STD_LOGIC;
          Q : inout STD_LOGIC;
          Q_n : inout STD_LOGIC);
end SR_Latch;

architecture SR_Latch_arch of SR_Latch is
begin
    process (S,R,Q,Q_n)
    begin
        Q <= R NOR Q_n;
        Q_n <= S NOR Q;
    end process;

end SR_Latch_arch;
```

-- <http://vhdlbbynaresh.blogspot.com.es/2013/07/design-of-sr-latch-using-behavior.html>

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity SR_Latch is
    port(
        enable : in STD_LOGIC;
        s : in STD_LOGIC;
        r : in STD_LOGIC;
        reset : in STD_LOGIC;
        q : out STD_LOGIC;
        qb : out STD_LOGIC
    );
end SR_Latch;

architecture SR_Latch_arc of SR_Latch is
begin

    latch : process (s,r,enable,reset) is
```


```

begin
    if (reset='1') then
        q <= '0';
        qb <= '1';
    elsif (enable='1') then
        if (s/=r) then
            q <= s;
            qb <= r;
        elsif (s='1' and r='1') then
            q <= 'Z';
            qb <= 'Z';
        end if;
    end if;
end process latch;

end SR_Latch_arc;

```

5.2.1 Basic D Flip Flop (FD)

 

CLK	D	Q_{next}
^	0	0
^	1	1
0	X	Q
1	X	Q

5.2.1.1 Code

-- Basic D Flip Flop

```

library IEEE;
use IEEE.std_logic_1164.all;

entity DFlipFlop is
    port(
        D : in std_logic;
        C : in std_logic;
        Q : out std_logic
    );
end DFlipFlop;

```

Architecture Behavioral of DFlipFlop is

```

begin
    process(C)
    begin
        if rising_edge(C) then
            Q <= D;
        end if;
    end process;
end Behavioral;

```

 


Figure 1: Synthesis Result

5.2.1.2 Synthesis results

- Target Device: xa3s500e-4cpg132
- Design Goal: Balanced

Logic Utilization	Used	Available	Utilization
Number of bonded IOBs	3	210	1%
Number of BUFG/BUFGCTRLs	1	32	3%

```

=====
*                               Final Report                               *
=====

Final Results
RTL Top Level Output File Name      : DFlipFlop.ngr
Top Level Output File Name          : DFlipFlop
Output Format                        : NGC
Optimization Goal                    : Speed
Keep Hierarchy                      : No

Design Statistics
# IOs                                : 3

Cell Usage :
# FlipFlops/Latches                  : 1
#      FD                            : 1
# Clock Buffers                      : 1
#      BUFGP                         : 1
# IO Buffers                         : 2
#      IBUF                          : 1
#      OBUF                          : 1
=====

```

Device utilization summary:

Selected Device : xa3s500ecpg132-4

Number of Slices:	0	out of	4656	0%
Number of IOs:	3			
Number of bonded IOBs:	3	out of	92	3%
IOB Flip Flops:	1			
Number of GCLKs:	1	out of	24	4%

5.2.1.3 Testbench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY tb IS
END tb;

ARCHITECTURE behavior OF tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT DFlipFlop
    PORT(
        D : IN  std_logic;
        C : IN  std_logic;
        Q : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal C : std_logic := '0';
    signal D : std_logic := '0';

    --Outputs
    signal Q : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: DFlipFlop PORT MAP (
        D => D,
        C => C,
        Q => Q
    );

    -- my clock process:
    clock : process(C)
    begin
        C <= not C after 20ns;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 110 ns;

        -- insert stimulus here
        D <= '1';
        wait for 90ns;
        D <= '0';
    end process;

```


```

        wait for 90ns;

        wait;
    end process;

END;

```

 

5.2.1.4 Simulation

5.2.2 D Flip Flop with Enable and Asynchronous Reset

5.2.2.1 Code

-- D Flip Flop with Enable and Asynchronous Reset

```

library IEEE;
use IEEE.std_logic_1164.all;

entity DFlipFlop is
    port(
        D : in std_logic; -- Data input
        C : in std_logic; -- Clock signal
        EN : in std_logic; -- Enable
        R : in std_logic; -- Asynchronous enable
        Q : out std_logic -- Data output
    );
end DFlipFlop;

```

Architecture Behavioral of DFlipFlop is

```

begin
    process(C, R) -- Only clock and asynchronous signals in the sensitivity list
    begin
        if R = '1' then
            Q <= '0';
        elsif rising_edge(C) then
            if EN = '1' then
                Q <= D;
            end if;
        end if;
    end process;
end Behavioral;

```

5.2.2.2 Synthesis XILINX primitive: FDCE, D Flip-Flop with Clock Enable and Asynchronous Clear

- Target Device: xa3s500e-4cpg132
- Design Goal: Balanced

Logic utilization	Used	Available	Utilization
Number of Slices	0	4656	0%

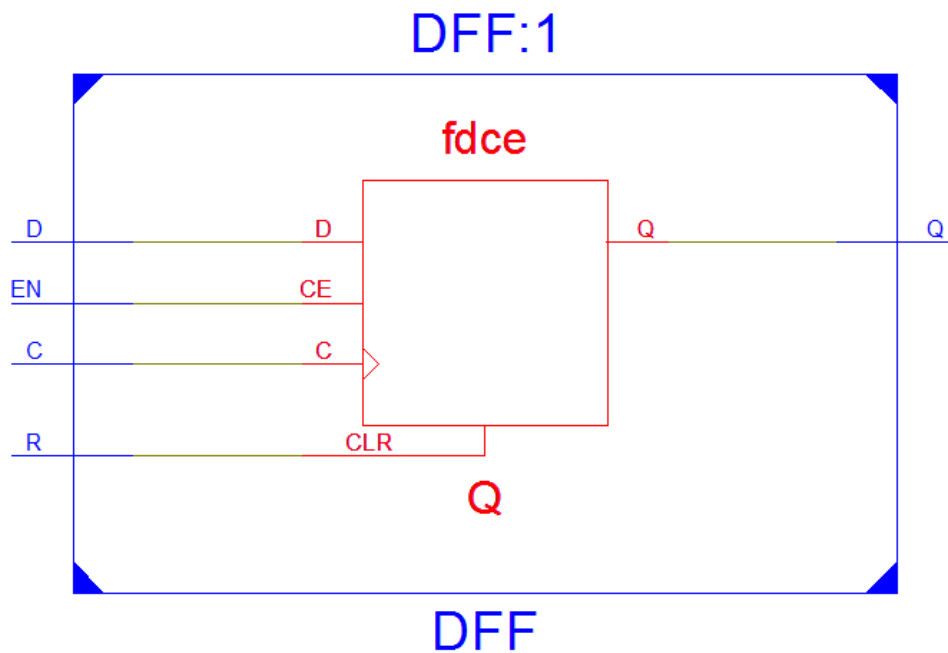


Figure 2: Synthesis Result

Number of bonded IOBs	5	92	5%
Number of GCLKs	1	24	4%

```
=====
*                               Final Report                               *
=====
```

Final Results

```
RTL Top Level Output File Name      : DFlipFlop.ngi
Top Level Output File Name          : DFlipFlop
Output Format                        : NGC
Optimization Goal                    : Speed
Keep Hierarchy                      : No
```

Design Statistics

```
# IOs                                : 5
```

Cell Usage :

```
# FlipFlops/Latches                  : 1
# FDCE                               : 1
# Clock Buffers                      : 1
# BUFGP                              : 1
# IO Buffers                         : 4
# IBUF                               : 3
# OBUF                               : 1
```

Device utilization summary:

Selected Device : xa3s500ecpg132-4

Number of Slices:	0	out of	4656	0%
Number of IOs:	5			
Number of bonded IOBs:	5	out of	92	5%
IOB Flip Flops:	1			
Number of GCLKs:	1	out of	24	4%

5.2.3 D Flip Flop with Enable, Reset and Preset

5.2.3.1 Code

```
-- Code from Wikibooks:
-- https://en.wikibooks.org/wiki/VHDL\_for\_FPGA\_Design/D\_Flip\_Flop

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DFF is
  port
  (
    clk : in std_logic;

    rst : in std_logic;
    pre : in std_logic;
    ce  : in std_logic;

    d : in std_logic;

    q : out std_logic
  );
end entity DFF;

architecture Behavioral of DFF is
begin
  process (clk) is
  begin
    if rising_edge(clk) then
      if (rst='1') then
        q <= '0';
      elsif (pre='1') then
        q <= '1';
      elsif (ce='1') then
        q <= d;
      end if;
    end if;
  end process;
end architecture Behavioral;
```

5.2.3.2 Synthesis Xilinx primitive: FDRSE

FDRSE is a single D-type flip-flop with synchronous reset (R), synchronous set (S), clock enable (CE) inputs. The reset (R) input, when High, overrides all other inputs and resets the Q output Low during the Low-to-High clock transition. (Reset has precedence over Set.) When the set (S) input is High and R is Low, the flip-flop is set, output High, during the Low-to-High clock (C) transition. Data on the D input is loaded into the flip-flop when R and S are Low and CE is High during the Low-to-High clock transition.

Inputs		Outputs			
R	S	CE	D	C	Q
1	X	X	X	?	0
0	1	X	X	?	1
0	0	0	X	X	No Change
0	0	1	1	?	1
0	0	1	0	?	0

5.3 FSM

FSM template

```
-- FSM template: from Circuit Design with VHDL

LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----
ENTITY <entity_name> IS
  PORT ( input: IN <data_type>;
         reset, clock: IN STD_LOGIC;
         output: OUT <data_type>);
END <entity_name>;
-----

ARCHITECTURE <arch_name> OF <entity_name> IS
  TYPE state IS (state0, state1, state2, state3, ...);
  SIGNAL pr_state, nx_state: state;
BEGIN
  ----- Lower section: -----
  PROCESS (reset, clock)
  BEGIN
    IF (reset='1') THEN
      pr_state <= state0;
    ELSIF (clock'EVENT AND clock='1') THEN
      pr_state <= nx_state;
    END IF;
  END PROCESS;
  ----- Upper section: -----
  PROCESS (input, pr_state)
  BEGIN
    CASE pr_state IS
      WHEN state0 =>
        IF (input = ...) THEN
          output <= <value>;
          nx_state <= state1;
        ELSE ...
          END IF;
      WHEN state1 =>
        IF (input = ...) THEN
          output <= <value>;
          nx_state <= state2;
        ELSE ...
          END IF;
      WHEN state2 =>
        IF (input = ...) THEN
          output <= <value>;
          nx_state <= state3;
        ELSE ...
          END IF;
    END CASE;
  END PROCESS;
END <arch_name>;
```

6 Examples

7 More