

# Rectifier Tables

Diego Trapero









## Table of contents







<b>1</b>	<b>Rectifier Tables</b>	<b>2</b>
1.1	Monophasic Uncontrolled Rectifiers with R load . . . . .	3
1.2	Monophasic Uncontrolled Full Wave Rectifier loads . . . . .	5
1.3	Monophasic Controlled Full Wave Rectifier, R vs RL load . . . . .	7
1.4	Triphasic Uncontrolled Rectifiers with R load . . . . .	9
1.5	Triphasic Controlled Half Wave Rectifier, R vs RL load . . . . .	11
1.6	Triphasic Controlled Full Wave Rectifier, R vs RL load . . . . .	13

# 1 Rectifier Tables
















1. Monophasic Uncontrolled Rectifiers with R load
2. Monophasic Uncontrolled Full Wave Rectifier loads
3. Monophasic Controlled Full Wave Rectifier, R vs RL load
4. Triphasic Uncontrolled Rectifiers with R load
5. Triphasic Controlled Half Wave Rectifier, R vs RL load
6. Triphasic Controlled Full Wave Rectifier, R vs RL load


## 1.1 Monophasic Uncontrolled Rectifiers with R load

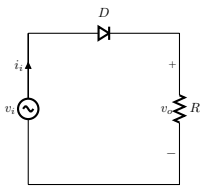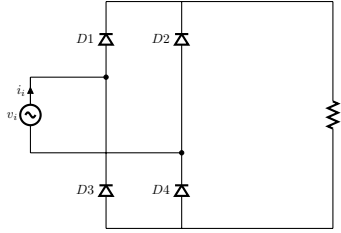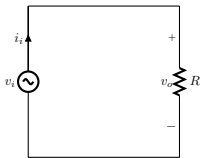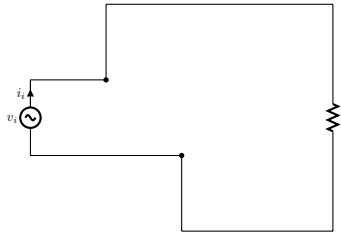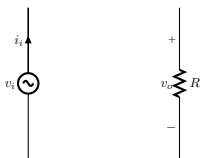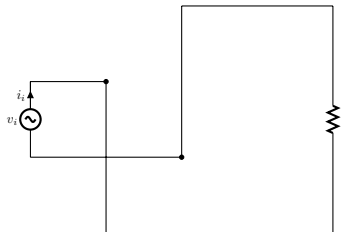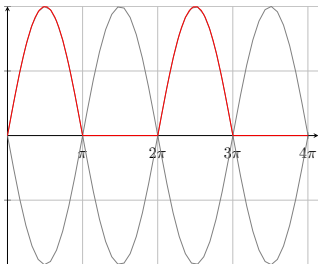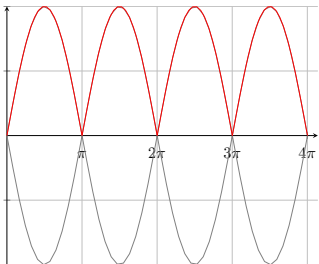What	Half Wave Rectifier	Full Wave Rectifier
Circuit Diagram		
$v_i > 0$ equivalent		
$v_i < 0$ equivalent		
Diode table		
$v_o$		
$\bar{v}_o$	$\bar{v}_o = \frac{V_{ip}}{\pi}$	$\bar{v}_o = \frac{2V_{ip}}{\pi}$

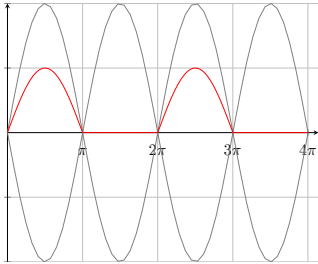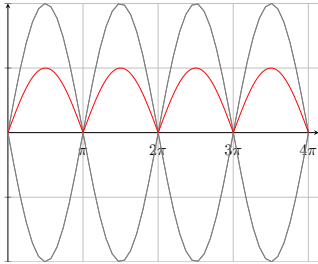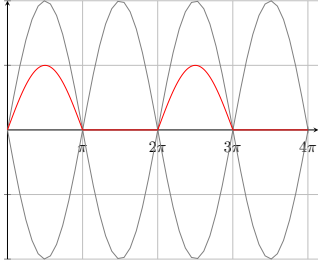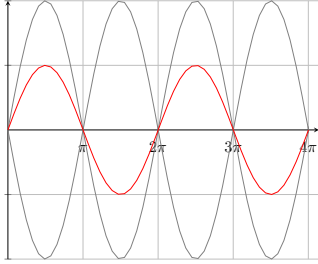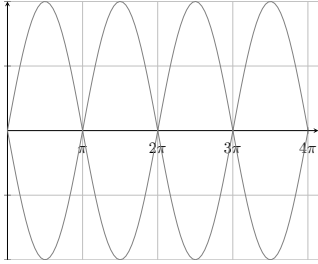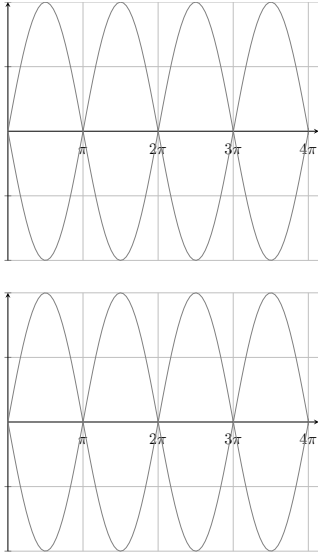$i_o = i_R$		
$i_i$		
Diodes Voltage $v_d$		





## 1.2 Monophasic Uncontrolled Full Wave Rectifier loads

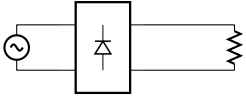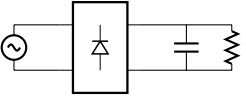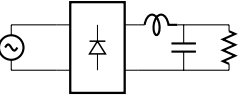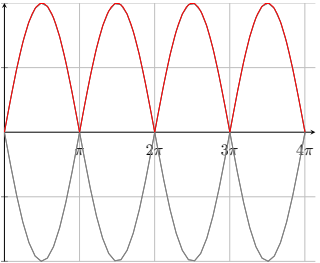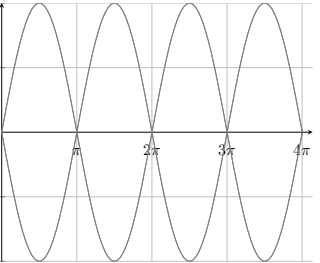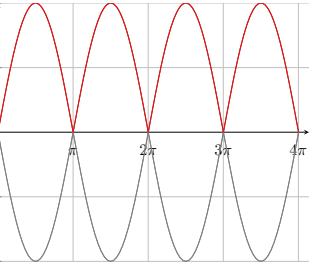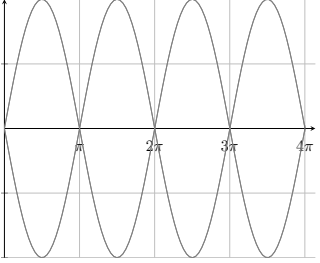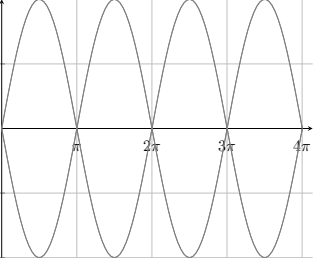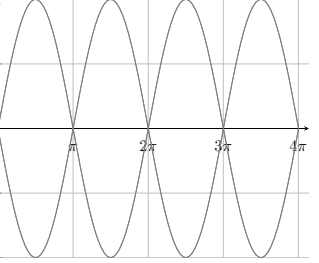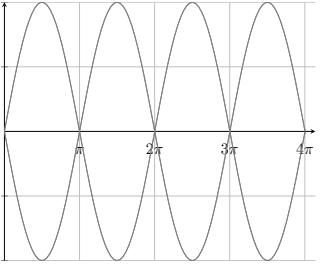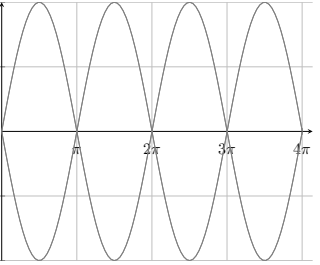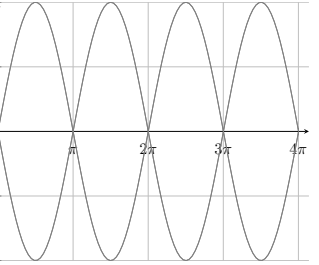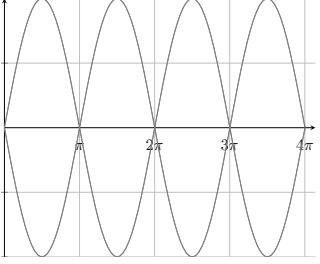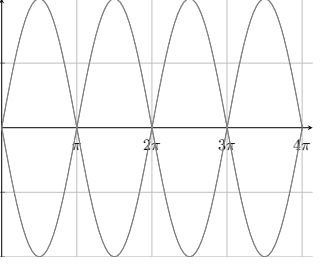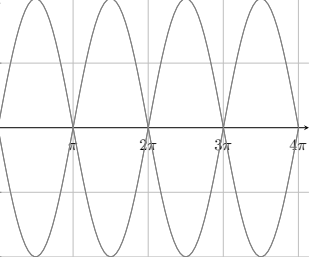What	R load	RC load	RLC load
Circuit Diagram			
$v_o$			
$v_R$			
$\bar{v}_R$			
$i_R$			
$i_o$			

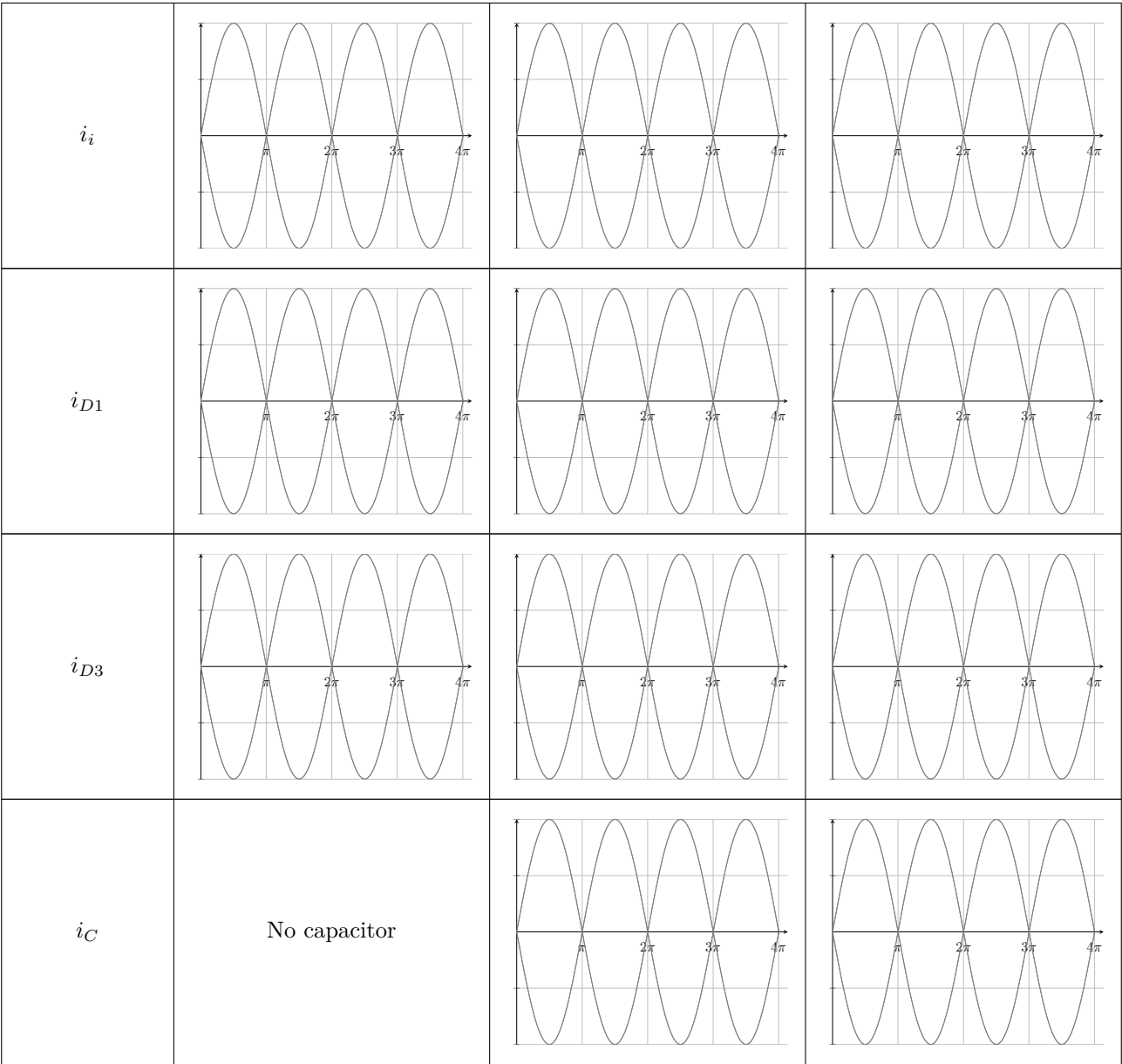





### 1.3 Monophasic Controlled Full Wave Rectifier, R vs RL load


What	Controlled FWR R load	Controlled FWR RL load
Circuit Diagram		
$v_o$		
$v_R$		
$\bar{v}_o(\alpha)$	$\bar{v}_o = \frac{V_i}{\pi} (\cos(\alpha) + 1)$	$\bar{v}_o = \frac{2V_i}{\pi} \cos(\alpha)$
Thyristor table		
$i_o(t)$		
$\bar{i}_o$		

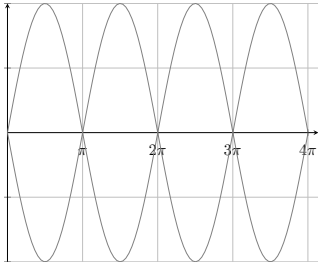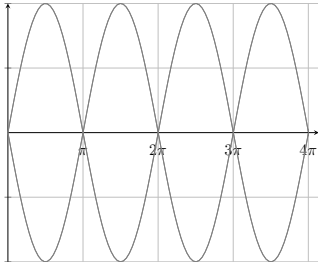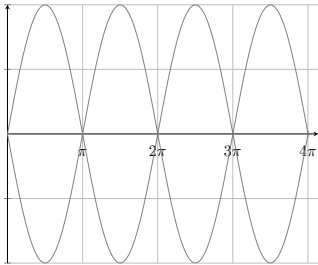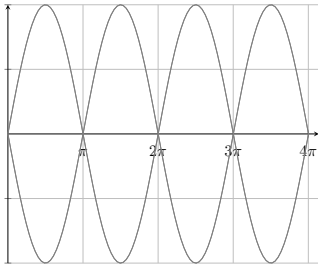$i_i(t)$		
$v_{T1}(t)$		
Power Factor		











## 1.4 Triphasic Uncontrolled Rectifiers with R load

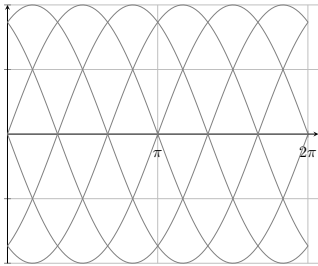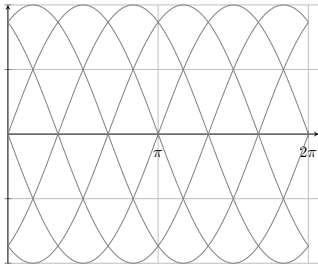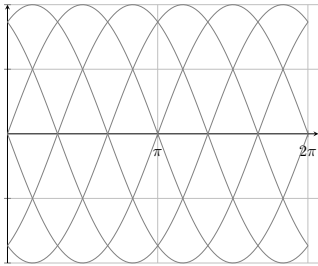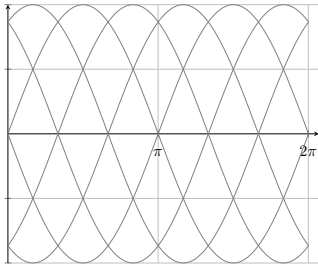What	3 $\Phi$ Half Wave Rectifier	3 $\Phi$ Full Wave Rectifier
Circuit Diagram		
$v_o$		
Peaks/period	3 peaks/period	3 peaks/period
Period	$\frac{2\pi}{3}$	$\frac{2\pi}{6} = \frac{\pi}{3}$
Integration limits	$\frac{\pi}{6}, \frac{5\pi}{6}$	
Load Voltage	Phase Voltage	Line Voltage
$\bar{v}_o$		
Diode table		
$i_o$		




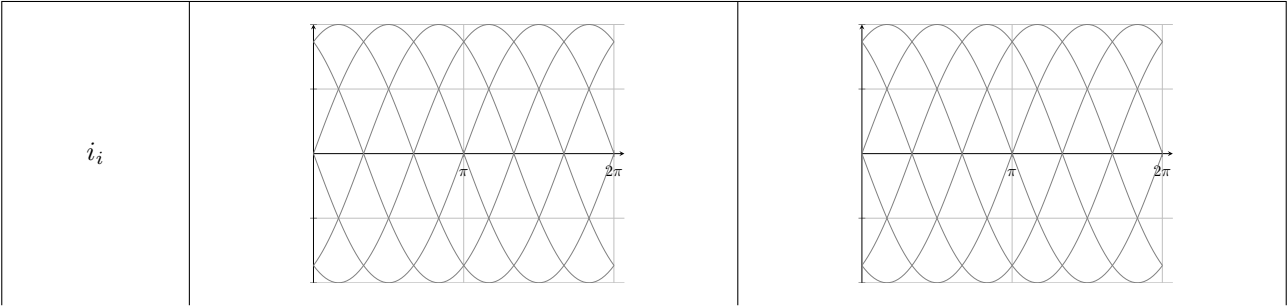


## 1.5 Triphasic Controlled Half Wave Rectifier, R vs RL load

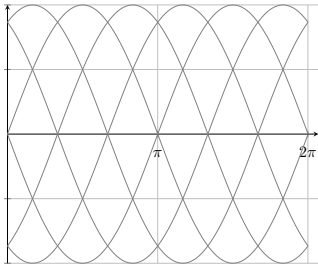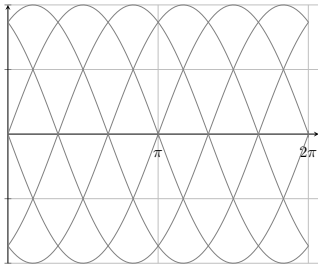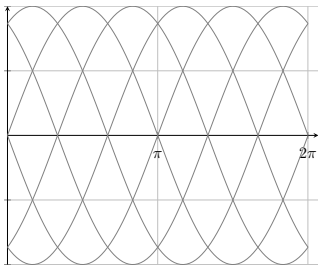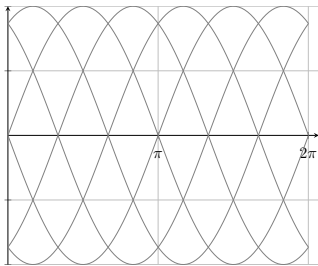What	3 $\Phi$ Controlled HWR R load	3 $\Phi$ Controlled HWR R load
Circuit Diagram		
$v_o$		
$v_R$		
Peaks/period	3 peaks/period	3 peaks/period
Period		
Integration limits		
Load Voltage		
$\bar{v}_o(\alpha)$		
Thyristor table		

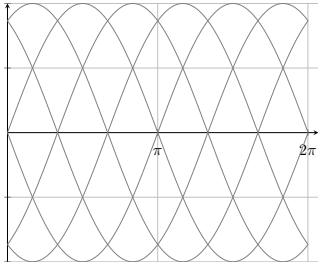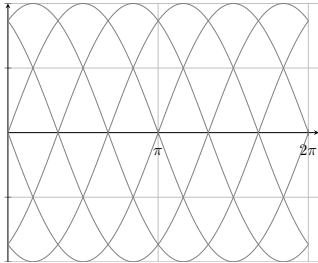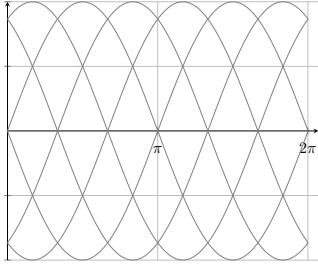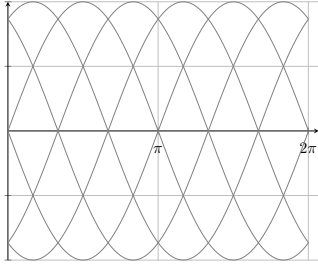$i_o$		
$i_i$		

## 1.6 Triphasic Controlled Full Wave Rectifier, R vs RL load

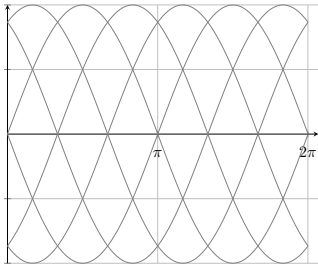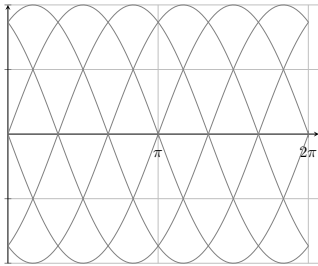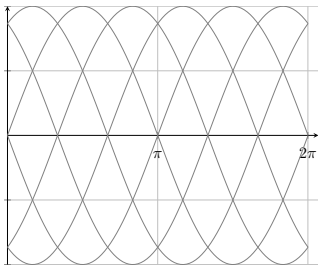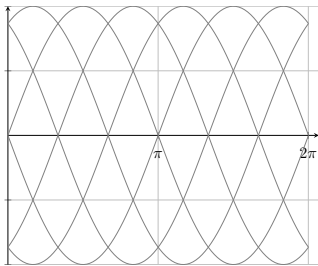What	3 $\Phi$ Controlled FWR R load	3 $\Phi$ Controlled FWR R load
Circuit Diagram		
$v_o$		
$v_R$		
Peaks/period	6 peaks/period	6 peaks/period
Period		
Integration limits		
Load Voltage		
$\bar{v}_o(\alpha)$		
Thyristor table		

