

# AC Cheatsheet

Diego Trapero

## Table of contents

<b>1</b>	<b>AC Cheatsheet</b>	<b>2</b>
1.1	Sinusoidal signal . . . . .	2
1.2	Phasors and complex numbers . . . . .	2
1.2.1	Phasor . . . . .	2
1.2.2	Generalized Ohm Law, complex impedance . . . . .	2
1.3	AC Power . . . . .	3

# 1 AC Cheatsheet

## 1 Sinusoidal signal

A sinusoidal signal in AC takes the form

$$s(t) = \sqrt{2}A \cdot \cos(\omega t + \varphi)$$

where

- $A \equiv A_{RMS}$  is the RMS value of the signal
- $\omega$  is the angular frequency,  $\omega = 2\pi f$  [rad]
- Frequency,  $f = \omega/2\pi$
- Period,  $T = 1/f$
- Amplitude of the signal is  $A/\sqrt{2}$

*Note:* In AC the sinusoidal function amplitude is taken as  $A/\sqrt{2}$ , so  $A$  is the RMS value of the signal. This way, we can directly use the RMS values of the signals to make calculations with power.

### Average and RMS values

- Average value:  $S_{AVG} = 0$
- RMS value:  $S_{RMS} = A$

## 1 Phasors and complex numbers

### 1 Phasor

$$s(t) = \sqrt{2}A \cdot \cos(\omega t + \varphi) \rightarrow \mathbf{S} = A\angle\varphi$$

In physics and engineering, a phase vector, or phasor, is a representation of a sinusoidal function whose amplitude, frequency, and phase are time-invariant

Euler's formula indicates that sinusoids can be represented mathematically by the sum of two complex-valued functions:

$$A \cdot \cos(\omega t + \theta) = A \cdot \frac{e^{i(\omega t + \theta)} + e^{-i(\omega t + \theta)}}{2}$$

or by the real part of one of the functions:

$$A \cdot \cos(\omega t + \theta) = \operatorname{Re} \left\{ A \cdot e^{i(\omega t + \theta)} \right\} = \operatorname{Re} \left\{ A e^{i\theta} \cdot e^{i\omega t} \right\}.$$

The term phasor can refer to either  $A e^{i\theta} e^{i\omega t}$  or just the complex constant,  $A e^{i\theta}$ . In the latter case, it is understood to be a shorthand notation, encoding the amplitude and phase of an underlying sinusoid.

An even more compact shorthand is angle notation:  $A\angle\theta$ .

## 1 Generalized Ohm Law, complex impedance

The **Generalized Ohm Law**:

$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$


where  $\mathbf{Z}$  is

- $\mathbf{Z} = R$  for resistors
- $\mathbf{Z} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$  for capacitors
- $\mathbf{Z} = j\omega L$  for inductors

## 1 AC Power
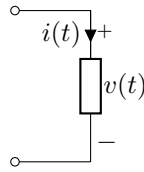
### Power in a two-terminal component

- Voltage:  $v(t) = \sqrt{2}V \cdot \cos(\omega t)$  ( $\varphi = 0$  because it's the reference)
- Current:  $i(t) = \sqrt{2}I \cdot \cos(\omega t - \varphi)$



### Instantaneous power

1. Instantaneous power definition

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= \sqrt{2}V \cos(\omega t) \cdot \sqrt{2}I \cos(\omega t - \varphi) \\ &= 2VI \cos(\omega t) \cos(\omega t - \varphi) \end{aligned}$$

2. Transform into sum of cosines using the identity  $\cos(a \cdot b) = \frac{1}{2}[\cos(a + b) + \cos(a - b)]$

$$\begin{aligned} p(t) &= 2VI \cdot \frac{1}{2}[\cos(\cancel{\omega t} - \cancel{\omega t} + \varphi) + \cos(\omega t + \omega t - \varphi)] \\ &= VI[\cos(\varphi) + \cos(2\omega t - \varphi)] \\ &= VI \cos(\varphi) + VI \cos(2\omega t - \varphi) \end{aligned}$$

The instantaneous power in an AC component is:

$$p(t) = VI \cos(\varphi) + VI \cos(2\omega t - \varphi)$$

We observe

- Power in the component has a constant term  $VI \cos(\varphi)$  and a fluctuating term that varies with time  $VI \cos(2\omega t - \varphi)$ .

### Average power

The instantaneous power is  $p(t) = VI \cos(\varphi) + VI \cos(2\omega t - \varphi)$ , so we can calculate the average power using the definition:

$$\bar{p}(t) = \text{integral} VI \cos(\varphi) + VI \cos(2\omega t - \varphi)$$

### Active and reactive power

- Active power:  $P = VI \cos(\varphi)$
- Reactive power:  $Q = VI \sin(\varphi)$

### Complex and apparent power

- Complex power is the complex number  $\mathbf{S} = \mathbf{VI}^* = P + Qj$
- Apparent power is the module of the complex power,  $S = VI$

**Power factor**

$$PF = \frac{P}{S}$$

$$PF = \cos(\varphi)$$

**AC power in a resistor**

$$P = VI$$

$$Q = 0$$

**Power in a inductor**

**Power in a capacitor**