

# Rectifier Tables: Monophasic Controlled

Diego Trapero

## Table of contents





|          |   |          |
|----------|---|----------|
| <b>1</b> | <b>Rectifier Tables</b>   | <b>2</b> |
| 1.1      | Monophasic Controlled Full Wave Rectifier, R vs RL load . . . . . | 3        |

# 1 Rectifier Tables

1. Monophasic Uncontrolled Rectifiers with R load
2. Monophasic Uncontrolled Full Wave Rectifier loads
3. **Monophasic Controlled Full Wave Rectifier, R vs RL load**
4. Triphasic Uncontrolled Rectifiers with R load
5. Triphasic Controlled Half Wave Rectifier, R vs RL load
6. Triphasic Controlled Full Wave Rectifier, R vs RL load

## 1.1 Monophasic Controlled Full Wave Rectifier, R vs RL load

| What                | Controlled FWR R load  | Controlled FWR RL load  |
|---------------------|--|---|
| Circuit Diagram     |  |   |
| $v_o$               |  |   |
| $\bar{v}_o(\alpha)$ | $\bar{v}_o = \frac{V_i}{\pi} (\cos(\alpha) + 1)$                                 | $\bar{v}_o = \frac{2V_i}{\pi} \cos(\alpha)$                                 |
| $v_R$               |  |   |
| Thyristor table     |  |   |
| $i_o(t)$            |  |   |
| $\bar{i}_o$         | $\bar{i}_o = \frac{\bar{v}_o}{R} = \frac{V_i}{\pi} \frac{(\cos(\alpha) + 1)}{R}$ | $\bar{i}_o = \frac{\bar{v}_o}{R} = \frac{2V_i}{\pi} \frac{\cos(\alpha)}{R}$ |
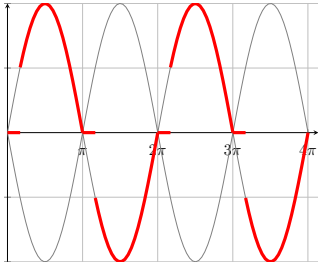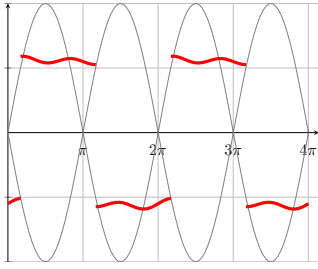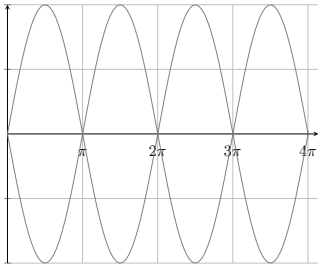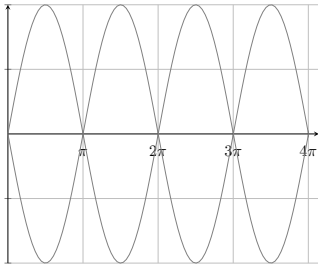
|                |   |   |
|----------------|---|---|
| $i_i(t)$       |  |                            |
| $v_{T1}(t)$    |  |                            |
| Power          |   | $P = V_{1 \text{ RMS}} I_{1 \text{ RMS}} \cos(\varphi_1)$ $P = V_{ip} I_o \frac{2\sqrt{2}}{\pi} \cos(\alpha)$ |
| Apparent Power |   | $S = V_{\text{RMS}} I_{\text{RMS}}$ $S = \frac{V_{ip}}{\sqrt{2}} I_o$   |
| Power factor   |   | $\text{PF} = \frac{2\sqrt{2}}{\pi} \cos(\alpha)$  |