

# Rectifier Tables: Triphasic Controlled

Diego Trapero





## Table of contents


<b>1</b>	<b>Rectifier Tables</b>	<b>2</b>
1.1	Triphasic Controlled Half Wave Rectifier, R vs RL load . . . . .	3
1.2	Triphasic Controlled Full Wave Rectifier, R vs RL load . . . . .	5

# 1 Rectifier Tables





1. Monophasic Uncontrolled Rectifiers with R load
2. Monophasic Uncontrolled Full Wave Rectifier loads
3. Monophasic Controlled Full Wave Rectifier, R vs RL load
4. Triphasic Uncontrolled Rectifiers with R load
5. **Triphasic Controlled Half Wave Rectifier, R vs RL load**
6. **Triphasic Controlled Full Wave Rectifier, R vs RL load**



## 1.1 Triphasic Controlled Half Wave Rectifier, R vs RL load

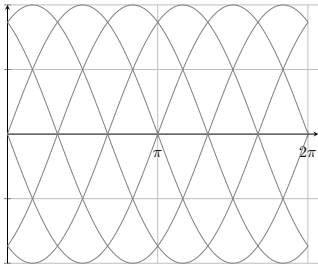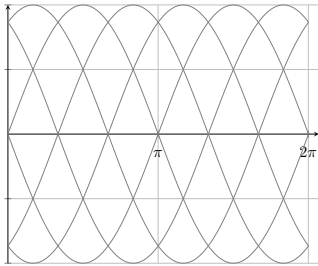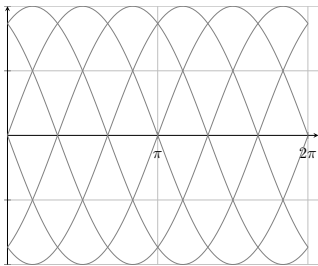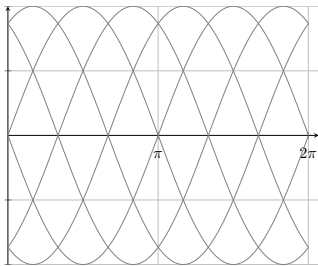What	3 $\Phi$ Controlled HWR R load	3 $\Phi$ Controlled HWR RL load
Circuit Diagram		
$v_o$		
$v_R$		
Peaks/period	3 peaks/period	3 peaks/period
Period		
Integration limits		
Load Voltage		
$\bar{v}_o(\alpha)$		$\bar{v}_o = \frac{1}{\frac{2\pi}{3}} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_{PN} \sin(\theta) d\theta$ $\bar{v}_o = \frac{3V_{PN}}{2\pi} [-\cos(\theta)]_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha}$ $\bar{v}_o = \frac{3\sqrt{3}}{2\pi} V_{PN} \cos(\alpha)$
Thyristor table		

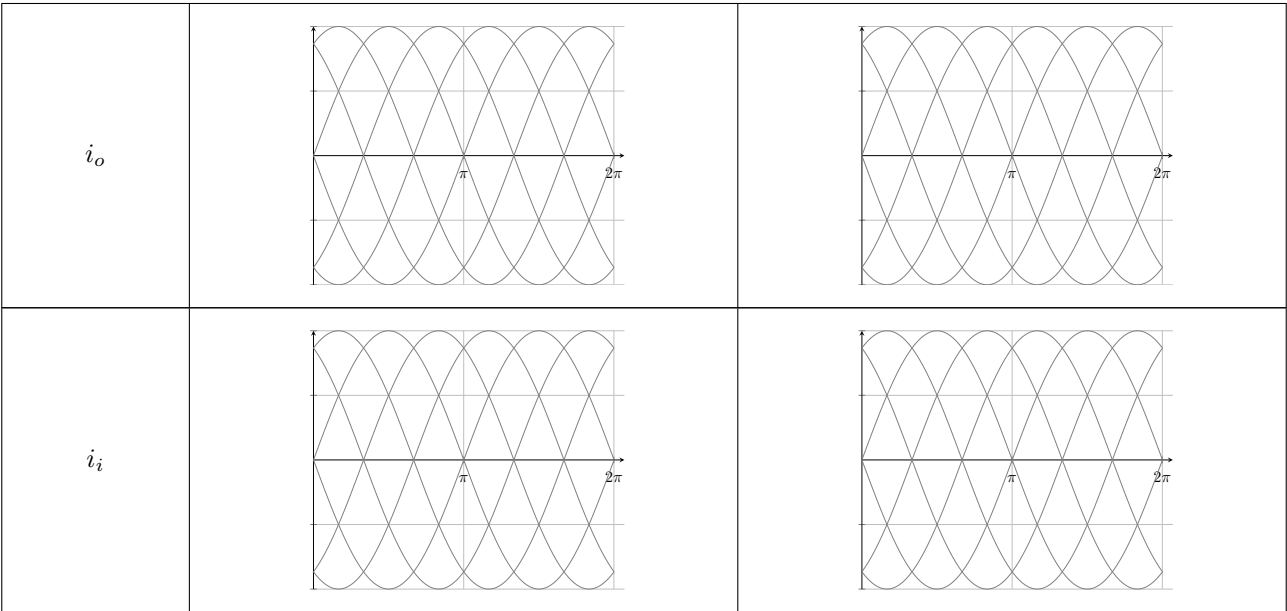

## 1.2 Triphasic Controlled Full Wave Rectifier, R vs RL load

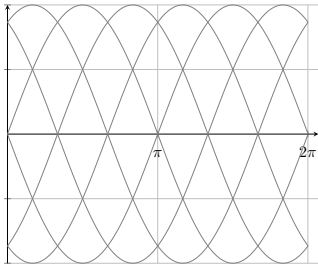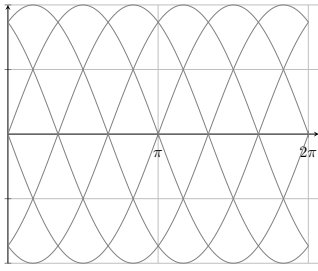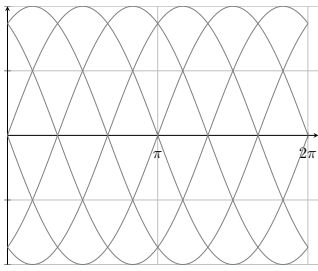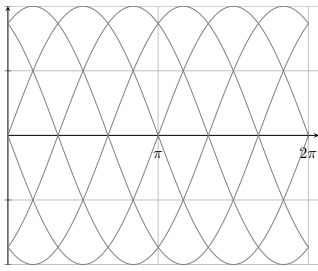What	3 $\Phi$ Controlled FWR R load	3 $\Phi$ Controlled FWR R load
Circuit Diagram		
$v_o$		
$v_R$		
Peaks/period	6 peaks/period	6 peaks/period
Period		
Integration limits		
Load Voltage		
$\bar{v}_o(\alpha)$		$\bar{v}_o = \frac{1}{\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} V_{LL} \sin(\theta) d\theta$ $\bar{v}_o = \frac{3V_{LL}}{\pi} [-\cos(\theta)]_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha}$ $\bar{v}_o = \frac{3}{\pi} V_{LL} \cos(\alpha)$
Thyristor table		

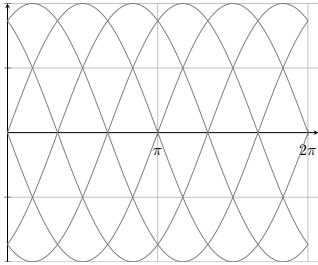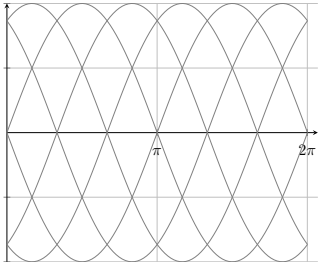$i_o$		
$i_i$	