

VHDL

Diego Trapero

Table of contents

1	VHDL syntax	2
1.1	when / else : concurrent signal assignment statement	2
1.2	Snippets	2
2	VHDL component	3
2.1	Gates	3
2.2	Biestables	3
2.3	FSM	7
3	Examples	8
4	More	8

1 VHDL syntax

1.1 when / else : concurrent signal assignment statement

A sequential signal assignment statement is also a concurrent signal assignment statement. Additional control is provided by the use of postponed and guarded.

```
[ label : ] sequential signal assignment statement  
  
[ label : ] [ postponed ] conditional_signal_assignment_statement ;  
  
[ label : ] [ postponed ] selected_signal_assignment_statement ;
```

The optional guarded causes the statement to be executed when the guarded signal changes from False to True. conditional signal assignment statement

A conditional assignment statement is also a concurrent signal assignment statement.

```
target <= waveform when choice; -- choice is a boolean expression  
target <= waveform when choice else waveform;  
  
sig <= a_sig when count>7;  
sig2 <= not a_sig after 1 ns when ctl='1' else b_sig;  
  
-- "waveform" for this statement seems to include [ delay_mechanism ]  
-- See sequential signal assignment statement
```

1.2 Snippets

Proceso de reloj útil para un testbench

```
--proceso de reloj, útil para un testbench  
  
-- inicializar la variable en la zona de señales  
SIGNAL CLK : STD_LOGIC := '0';  
  
clock : process(clk)  
begin  
    clk <= not clk after 20ns;  
end process;
```

Todos los procesos sincronos con resets

```
--todos los procesos sincronos con resets:  
  
process (clk, reset)  
    if reset = '1' then  
        -- do RESET, other asynchronous taska ;  
    elseif rising_edge(clk) then  
        -- SINCRONOUS TASKS  
        if enable = '1' then  
            -- ENABLED TASKS  
        end if;  
    end if;  
end process;
```

2 VHDL component

2.1 Gates

NAND Gate

```
entity NANDGate is
  port (
    a, b : in bit;
    x : out bit
  );
end NANDGate;

architecture NANDArch of NANDGate is
begin
  x <= a NAND b;
end NANDArch;
```

2.2 Biestables

Latch Internal signal implementation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity S_R_latch_top is
  Port ( S : in    STD_LOGIC;
         R : in    STD_LOGIC;
         Q : out   STD_LOGIC);
end S_R_latch_top;

architecture Behavioral of S_R_latch_top is
  signal Q2    : STD_LOGIC;
  signal notQ  : STD_LOGIC;
begin

  Q    <= Q2;
  Q2   <= R nor notQ;
  notQ <= S nor Q2;

end Behavioral;
```

Latch Inout ports implementation

```
entity SR_Latch is
  Port ( S,R : in  STD_LOGIC;
         Q : inout STD_LOGIC;
         Q_n : inout STD_LOGIC);
end SR_Latch;

architecture SR_Latch_arch of SR_Latch is
begin
  process (S,R,Q,Q_n)
  begin
    Q <= R NOR Q_n;
    Q_n <= S NOR Q;
  end process;

end SR_Latch_arch;
```

-- <http://vhdlbbynaresh.blogspot.com.es/2013/07/design-of-sr-latch-using-behavior.html>

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity SR_Latch is
    port(
        enable : in STD_LOGIC;
        s : in STD_LOGIC;
        r : in STD_LOGIC;
        reset : in STD_LOGIC;
        q : out STD_LOGIC;
        qb : out STD_LOGIC
    );
end SR_Latch;

architecture SR_Latch_arc of SR_Latch is
begin

    latch : process (s,r,enable,reset) is
    begin
        if (reset='1') then
            q <= '0';
            qb <= '1';
        elsif (enable='1') then
            if (s/=r) then
                q <= s;
                qb <= r;
            elsif (s='1' and r='1') then
                q <= 'Z';
                qb <= 'Z';
            end if;
        end if;
    end process latch;

end SR_Latch_arc;
```

D Flip-Flop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DFF is
    port(
        D : in std_logic; --Data input
        C : in std_logic; --Clock signal
        Q : out std_logic --Data output
    );
end DFF;

architecture Behavioral of DFF is

begin
    process(C)
    begin
        if rising_edge(C) then
            Q <= D;
        end if;
    end process;
end Behavioral;
```

D Flip Flop with Enable and Reset

 


Figure 1: Synthesis Result

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity DFF is
    port(
        D : in  std_logic; --Data input
        C : in  std_logic; --Clock signal
        EN : in  std_logic; --Enable signal
        R : in  std_logic; -- Asynchronous reset
        Q : out std_logic  --Data output
    );
end DFF;

architecture Behavioral of DFF is
begin

    process(C, R)
    begin
        if (R = '1') then
            Q <= '0';
        else if rising_edge(C) AND EN='1' then
            Q <= D;
        end if;
        end if;
    end process;

end Behavioral;

```

D Flip Flop with Enable, Reset and Preset

 


Figure 2: Synthesis Result

-- Code from Wikibooks:
 -- https://en.wikibooks.org/wiki/VHDL_for_FPGA_Design/D_Flip_Flop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DFF is
  port
  (
    clk : in std_logic;

    rst : in std_logic;
    pre : in std_logic;
    ce : in std_logic;

    d : in std_logic;

    q : out std_logic
  );
end entity DFF;

architecture Behavioral of DFF is
begin
  process (clk) is
  begin
    if rising_edge(clk) then
      if (rst='1') then
        q <= '0';
      elsif (pre='1') then
        q <= '1';
      elsif (ce='1') then
        q <= d;
      end if;
    end if;
  end process;
end architecture Behavioral;
```

With Guarded Block

-- D Flip Flop with Guarded Block, from Circuit Design with VHDL

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
  PORT (
    d, clk, rst: IN STD_LOGIC;
    q : out std_logic
  );
END dff;

ARCHITECTURE dff OF dff IS
BEGIN
  b1: BLOCK (clk'EVENT AND clk='1')
  BEGIN
    q <= GUARDED '0' WHEN rst='1' ELSE d;
  END BLOCK b1;
END dff;
```

2.3 FSM

FSM template

-- FSM template: from Circuit Design with VHDL

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----
ENTITY <entity_name> IS
  PORT ( input: IN <data_type>;
    reset, clock: IN STD_LOGIC;
    output: OUT <data_type>);
END <entity_name>;
-----

ARCHITECTURE <arch_name> OF <entity_name> IS
  TYPE state IS (state0, state1, state2, state3, ...);
  SIGNAL pr_state, nx_state: state;
BEGIN
  ----- Lower section: -----
  PROCESS (reset, clock)
  BEGIN
    IF (reset='1') THEN
      pr_state <= state0;
    ELSIF (clock'EVENT AND clock='1') THEN
      pr_state <= nx_state;
    END IF;
  END PROCESS;
  ----- Upper section: -----
  PROCESS (input, pr_state)
  BEGIN
    CASE pr_state IS
      WHEN state0 =>
        IF (input = ...) THEN
          output <= <value>;
          nx_state <= state1;
        ELSE ...
          END IF;
      WHEN state1 =>
        IF (input = ...) THEN
          output <= <value>;
```

```
        nx_state <= state2;
ELSE ...
    END IF;
    WHEN state2 =>
        IF (input = ...) THEN
            output <= <value>;
            nx_state <= state3;
        ELSE ...
    END IF; ...
    END CASE;
    END PROCESS;
END <arch_name>;
```

3 Examples

4 More